



### Triple Choice Sound Effects

Build the circuit shown on the left and turn on the switch S1. Place a finger on top of the photoresistor (RP) to hear a second sound. With your finger still on RP, press the button on switch S2 to hear the third sound.

This circuit was created by Jacob from Wisconsin.