



Requires SC-500
or larger parts set.

Step By Step Adjustable Meter

Build the circuit shown on the left. When you move the adjustable resistor (RV) control lever left and right you create a walking sound in the speaker and make the meter pointer moves like it's walking.

This circuit was created by Connor
Joe from Wisconsin.