



Big Static

Build the circuit shown on the left. Add the two Jumper Wires, but don't snap them together. Tap the red and black wires together gently. You will hear a static sound on the speaker (SP).

This circuit was created by Philip.



WARNING: Do not keep the two jumper wires together. There is no sound when they are together, and this may damage the speaker.