



Meter and LED Combo

Use the LOW (or 10mA) setting on the meter (M2) and shine a light on the solar cell (B2). When the meter gets up to 10, if there's still more electricity, an LED will go on.

This circuit was created by Scott from Texas.

Requires SC-750 parts set.