



Requires SC-300
or larger parts set.

LED Selector

Moving the resistor (RV) up lights LED. If you move the resistor down then LED D2 lights.

This circuit was created by David
and Gary from California