



Requires SC-100
or larger parts set.

Two speed motor with lights

Build the circuit shown. Turn switch S1 on the LED D2 lights as the motor spins fast. Now press switch S2, the motor slows down as the lamp L1 lights and LED D2 turns off.

This circuit was created by
David