



Requires SC-300  
or larger parts set.

## Air Horn

This circuit is similar to project #275

Build the circuit shown. Set the control of the adjustable resistor (RV) to the far left side. Turn the circuit on using the slide switch (S1). Place the microphone (X1), in front of the speaker (SP). You will hear feed back that sounds like an air horn.

This circuit was created by  
Hunter from California