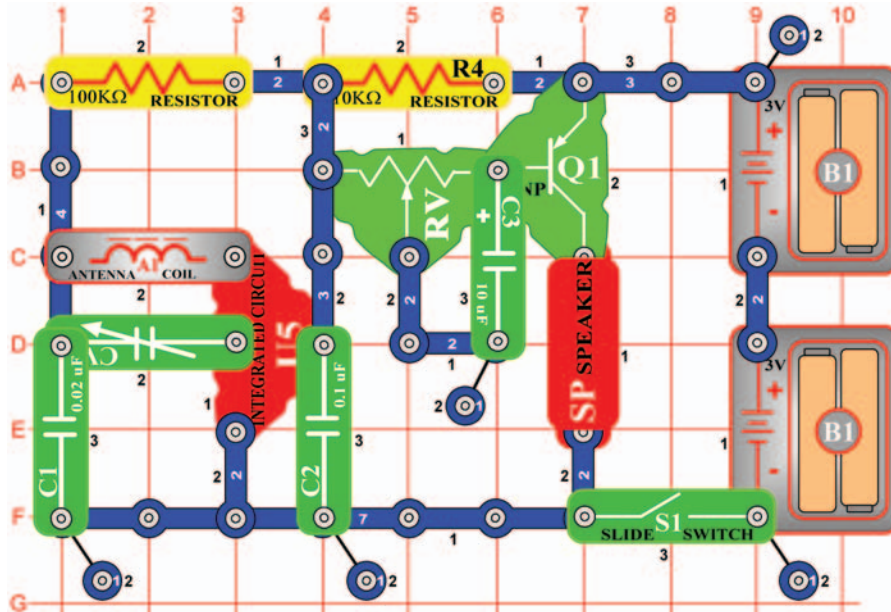


Project #A67

AM Radio

OBJECTIVE: To build a one IC AM radio.



Turn on the slide switch (S1) and adjust the variable capacitor (CV) for a radio station.

Requires SC-300 or larger parts set.